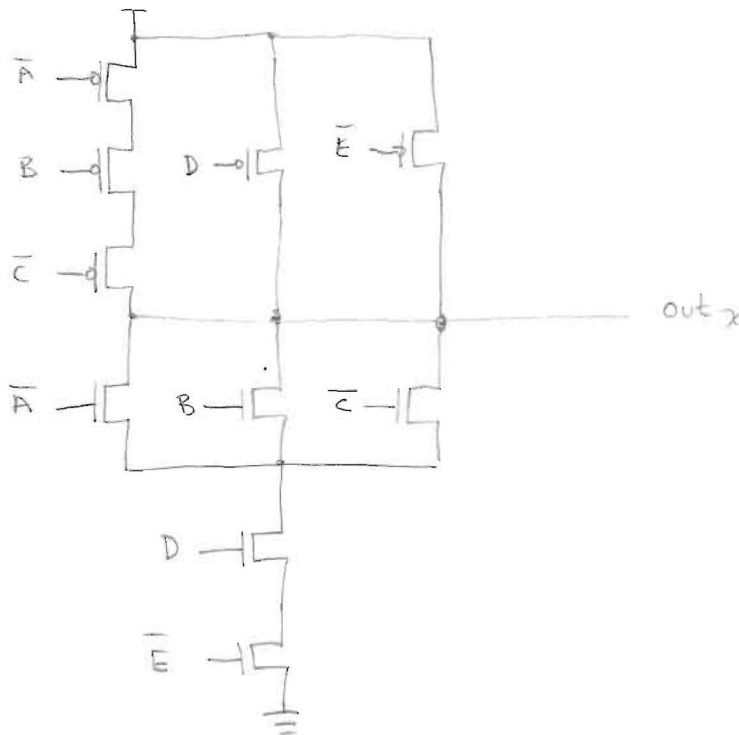


Show your work for any possible partial credit. 100 possible points, 8 exam pages plus two supplemental pages.

High Level Language		
Assembly Language		
Instruction Set		
Memory	Data Path	Controller
Storage	Functional Units	State Machines
Building Blocks		
Gate		
Switches and Wires		

1) (10 points) For the expression below, create a switch level implementation using N and P type switches. Assume both inputs and their complements are available. Your design should contain no shorts or floats. Implement the equation exactly as is (no simplifying).



$$\text{Out}_x = A \cdot \overline{B} \cdot C + \overline{D} + E$$



High Level Language		
Assembly Language		
Instruction Set		
Memory	Data Path	Controller
Storage	Functional Units	State Machines
Building Blocks		
Gate		
Switches and Wires		

  2) (10 points) Implement the following expression using only AND gates and inverters. Then determine the number of switches required. Use proper mixed logic notation. Do not modify the expression. Do not assume complements of inputs are available. You may use 3 input AND gates if needed.


$$\text{Out} = (G + \overline{H})(\overline{I \cdot J}) + K + \overline{L \cdot M}$$



6 AND x 6 + 9 inverters x 2

Number of switches 54

High Level Language		
Assembly Language		
Instruction Set		
Memory	Data Path	Controller
Storage	Functional Units	State Machines
Building Blocks		
Gate		
Switches and Wires		

 

3) (10 points) Implement a 2 to 4 decoder using AND gates and inverters, (you may use 3 input AND Gates). You must show a truth table, boolean equations for each of the four outputs, and then the implementation of the 2 to 4 decoder.


EN	I ₁	I ₀	O ₀	O ₁	O ₂	O ₃
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

$$O_0 = EN \cdot \overline{I_1} \cdot \overline{I_0}$$

$$O_1 = EN \cdot \overline{I_1} \cdot I_0$$


$$O_2 = EN \cdot I_1 \cdot \overline{I_0}$$

$$O_3 = EN \cdot I_1 \cdot I_0$$

 


High Level Language		
Assembly Language		
Instruction Set		
Memory	Data Path	Controller
Storage	Functional Units	State Machines
Building Blocks		
Gate		
Switches and Wires		

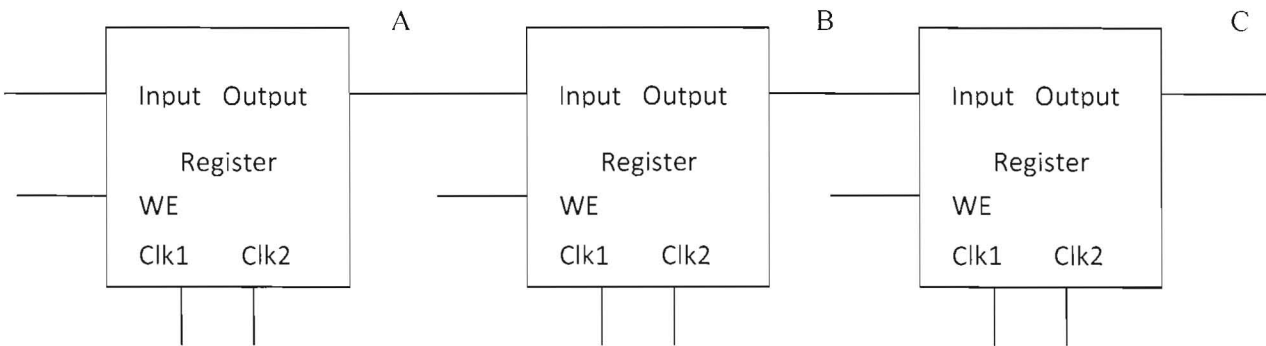
4) (10 points) Consider the register implementation below.



 
Assume the following signals are applied to the registers above. Draw the signal at point A (output of the first register), point B (output of the second register) and point C (output of the third register). Assume all stored signals are UNKNOWN at start.



High Level Language		
Assembly Language		
Instruction Set		
Memory	Data Path	Controller
Storage	Functional Units	State Machines
Building Blocks		
Gate		
Switches and Wires		

 


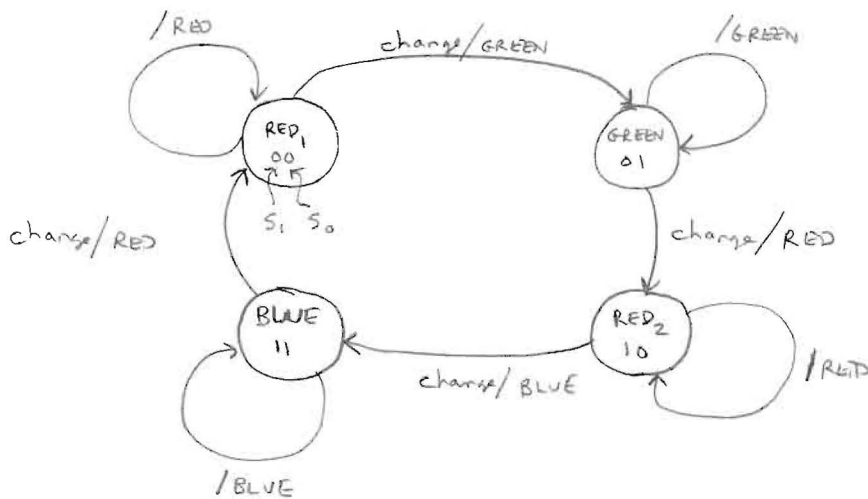5) (20 points total) Implement a state machine that outputs three signals names RED, GREEN, and BLUE and with the single input change. As long as change input is a high, the outputs go high one at a time in this specific order RED, GREEN, RED, BLUE, RED, GREEN ,RED, BLUE,however when the change input is a low, the output that is high at present stays high until the change input is set to a high. Draw a state diagram, show a state table, and show the complete and entire state machine design. You may use any type of logic gate you want.




CHANGE	S_1	S_0	NS_1	NS_0	RED	GREEN	BLUE
0	0	0	0	0	1	0	0
1	0	0	0	1	0	1	0
0	0	1	0	1	0	1	0
1	0	1	1	0	1	0	0
0	1	0	1	0	1	0	0
1	1	0	1	1	0	0	1
0	1	1	1	1	0	0	1
1	1	1	0	0	1	0	0


Blank work page for Problem 5

 

 
$$NSI = \text{change } \overline{S_1} S_0 + \text{change } S_1 + S_1 \overline{S_0}$$



 
$$NSO = \text{change } S_0 + \text{change } \overline{S_0}$$


 
$$RED = \text{change } S_0 + \text{change } \overline{S_0}$$



 
$$GREEN = \text{change } \overline{S_1} \overline{S_0} + \text{change } \overline{S_1} S_0$$



$$BLUE = \text{change } S_1 S_0 + \text{change } S_1 \overline{S_0}$$

Blank work page for Problem 5

 

High Level Language		
Assembly Language		
Instruction Set		
Memory	Data Path	Controller
Storage	Functional Units	State Machines
Building Blocks		
Gate		
Switches and Wires		

6) (10 points) Using the attached single cycle data path we have discussed extensively in class (see last pages of exam for part of it), using as few registers as possible, implement the microcode for the following operation

$$M[R5] = (R3 + 8 R2 + 5M[R4])/4$$

#	X	Y	Z	rw e	im en	im va	au en	-a /s	lu en	lf	su en	st	ld en	st en	r/ -w	msel	description
1	2	X	2	1	1	-3	0	X	0	XXXX	1	00	0	0	X	0	R2 = R2 LOGICAL SHIFT -3
2	2	3	3	1	0	X	1	0	0	XXXX	0	X	0	0	X	0	R3 = R3 + R2
3	4	X	2	1	0	X	0	X	0	XXXX	0	X	1	0	1	1	R2 = M[R4]
4	2	3	3	1	0	X	1	0	0	XXXX	0	X	0	0	X	0	R3 = R3 + R2
5	2	X	2	1	1	-2	0	X	0	XXXX	1	00	0	0	X	0	R2 = R2 LOGICAL SHIFT -2
6	2	3	3	1	0	X	1	0	0	XXXX	0	X	0	0	X	0	R3 = R3 + R2
7	3	X	3	1	1	+2	0	X	0	XXXX	1	01	0	0	X	0	R3 = R3 ARITHMETIC SHIFT +2
8	5	3	X	0	0	X	0	X	0	XXXX	0	X	0	1	0	1	M[R5] = R3
9																	

High Level Language		
Assembly Language		
Instruction Set		
Memory	Data Path	Controller
Storage	Functional Units	State Machines
Building Blocks		
Gate		
Switches and Wires		

7) (10 points) Instruction Format. Suppose you were designing a new computer with a 64 bit instruction word and a 64 bit addressed memory, 2048 different instructions, and 1024 registers. What are the number of bits required in each of the different required fields in the Register Format Instructions? (You may have more or less lines in the table below than you need).

Field Name	Minimum Number of bits required
OPCODE	11 BITS
Z	10 BITS
X	10 BITS
Y	10 BITS
TO BE DEFINED BITS	$64 - 41 = 23$

$$2048 \Rightarrow 2^{11}$$

$$1024 \Rightarrow 2^{10}$$


8) (20 points) MIPS Assembly language programming. Write a MIPS procedure named search that will take memory value starting at the location contained in register \$4 and search sequential memory locations until it finds the value negative one. Once it finds the value negative one in a memory location, put the address of the memory location that contains the negative one into register \$5 and return back to the program that called your procedure. You may need more or fewer rows in the tables below.

Label:	Instruction	Comment
SEARCH	addi \$6,\$0,-1	STORE -1 FOR COMPARISONS
repeat	lw \$7(\$4)	PUT FIRST MEMORY VALUE INTO \$7
	beq \$7,\$6,DONE	IF FOUND VALUE DONE
	addi \$4,\$4,4	INCREMENT \$4 BY 4 BYTES
	jmp repeat	KEEP DOING
DONE	add \$5,\$0,\$4	PUT CURRENT MEMORY ADDRESS IN \$5
	jr \$31	RETURN TO PC = \$31

Explain the use of ALL of the registers used in your code:

Register	Was used for the purposes of
\$4	Starting location of memory
\$5	Contains memory location where -1 was found
\$6	STORE -1 TO COMPARE TO
\$7	STORE EACH MEMORY VALUE TESTING

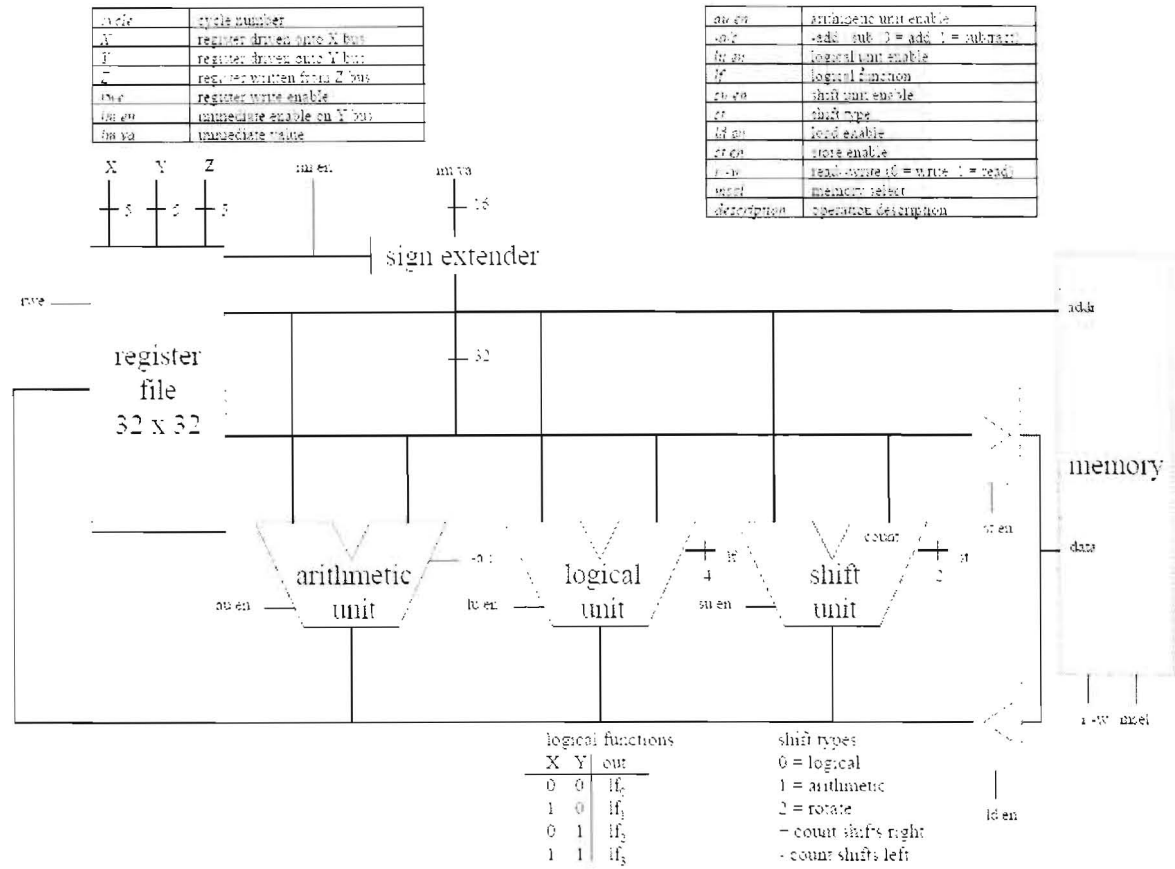You may tear off the following 2 pages from the exam and you do not need to turn in them in.



instruction	example	meaning
add	add R1, R2, R3	$R1 = R2 + R3$
subtract	sub R1, R2, R3	$R1 = R2 - R3$
add immediate	addi R1, R2, 100	$R1 = R2 + 100$
multiply	mul R1, R2, R3	$R1 = R2 * R3$
divide	div R1, R2, R3	$R1 = R2 / R3$
and	and R1, R2, R3	$R1 = R2 \& R3$
or	or R1, R2, R3	$R1 = R2 R3$
xor	xor R1, R2, R3	$R1 = R2 \oplus R3$
and immediate	andi R1, R2, 100	$R1 = R2 \& 100$
or immediate	ori R1, R2, 100	$R1 = R2 100$
xor immediate	xori R1, R2, 100	$R1 = R2 \oplus 100$
shift left logical	sll R1, R2, 5	$R1 = R2 \ll 5$ (logical)
shift right logical	srl R1, R2, 5	$R1 = R2 \gg 5$ (logical)
shift left arithmetic	sla R1, R2, 5	$R1 = R2 \ll 5$ (arithmetic)
shift right arithmetic	sra R1, R2, 5	$R1 = R2 \gg 5$ (arithmetic)
load word	lw R1, 100	$R1 = \text{memory}[100]$
store word	sw R1, 100	$\text{memory}[100] = R1$
load upper immediate	lui R1, 100	$R1 = 100 \ll 20$
branch if equal	bne R1, R2, 100	if $R1 = R2$, $PC = PC + 4$; else $PC = 100 + 4$
branch if not equal	bne R1, R2, 100	if $R1 = R2$, $PC = PC + 4$; else $PC = 100 + 4$
set if less than	slt R1, R2, R3	if $R2 < R3$, $R1 = 1$; else $R1 = 0$
set if less than immediate	slti R1, R2, 100	if $R2 < 100$, $R1 = 1$; else $R1 = 0$
jump	j 10000	$PC = 10000 + 4$
jump register	jr R31	$PC = R31$
jump and link	jral 10000	$R31 = PC + 4$; $PC = 10000 + 4$

K MAPS:

